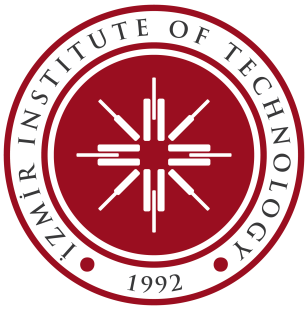


İzmir Institute of Technology

Faculty of Engineering

Department of Electrical and Electronics Engineering

EE 315 Electronics Laboratory Prelab Sheet

Experiment 2

Submitted By:

Baran Güvendiren - 310206029
Ozan İnan - 330206062
Mohammadhossein Nafaryeh - 320206059

October 16, 2026

1 LTspice Simulation

1.1 Full-Wave Bridge Rectifier

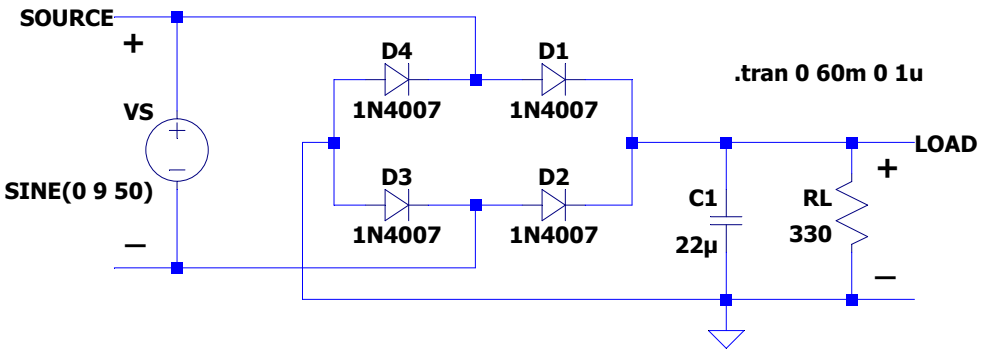


Figure 1: Schematic of full-wave bridge rectifier circuit

$V_{L,\text{peak}}$	f_L	**Number of conducting diodes**
7.59 V	100 Hz	2

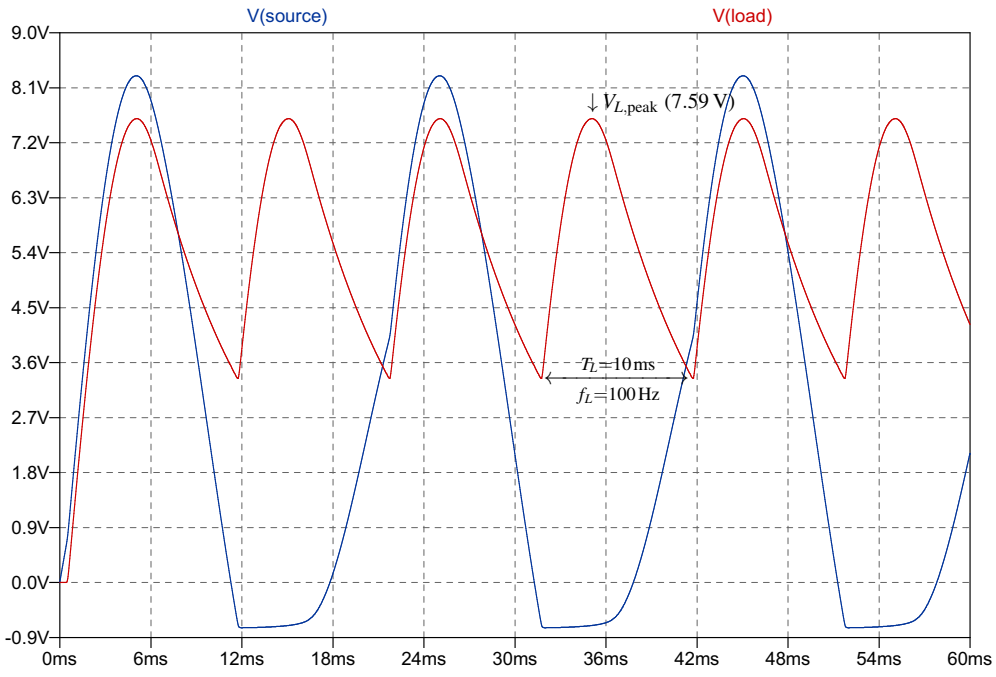


Figure 2: Input and output voltage waveforms of the full-wave bridge rectifier circuit

1.2 Zener Diode Regulator

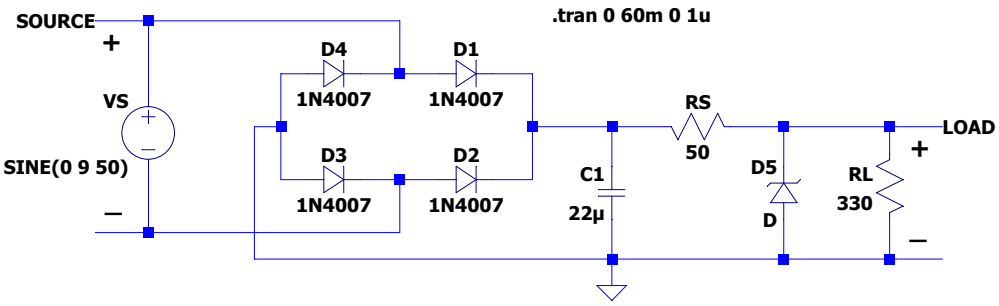


Figure 3: Schematic of Zener diode regulator circuit

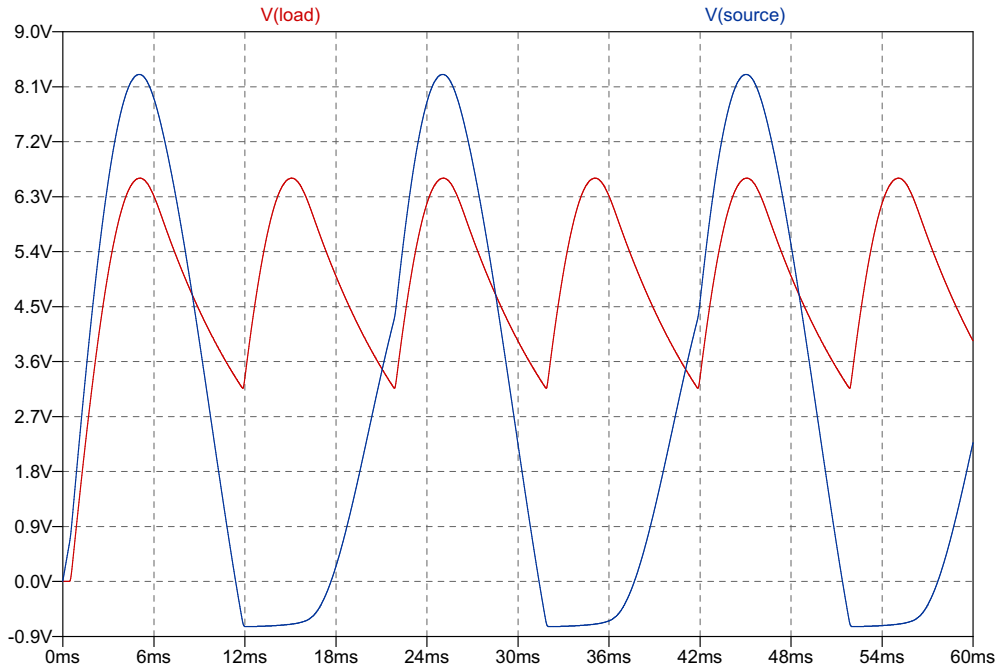


Figure 4: Input and output voltage waveforms of the Zener diode regulator circuit

$V_{o,DC}$	I_Z
TBC	TBC